


ECE 2300 Digital Logic and Computer Organization

Implementing the Note Player Control FSM

revision: 2025-10-15-20-53

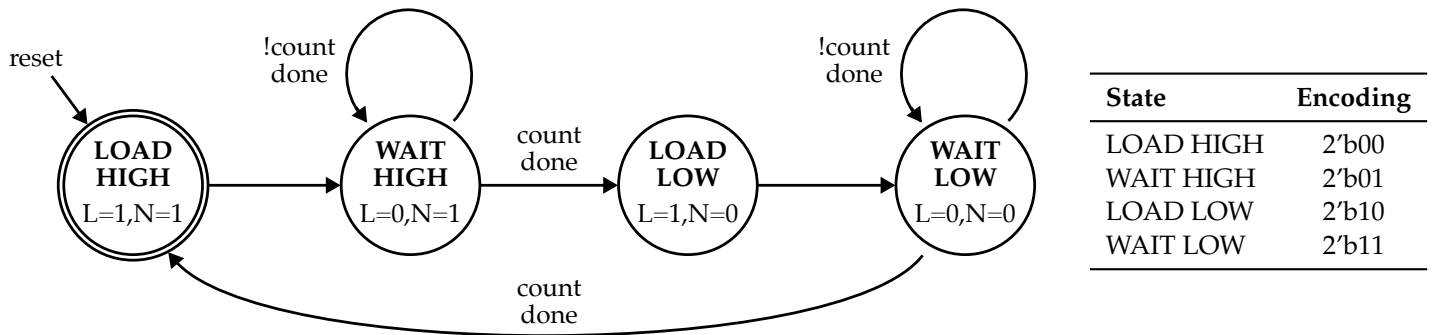Problem 1. FSM Next State and Output Table

Consider the following sequential finite-state machine and state encoding.



Fill in the following FSM next state and output table. D is the count done input. L is the count load output. N is the note output.

S_1	S_0	D	$S_{1,next}$	$S_{0,next}$	L	N
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

Problem 2. FSM Next State and Output Equations

Complete the Karnaugh maps below to derive a minimal sum-of-products (SOP) Boolean equation for each output. Each circle in your Karnaugh map must correspond exactly to the products in the minimal sum-of-products equation. Label each circle with the corresponding product and write the final minimal SOP equation.


	S1 S0			
D	00	01	11	10
0				
1				



	S1 S0			
D	00	01	11	10
0				
1				



	S1 S0			
D	00	01	11	10
0				
1				

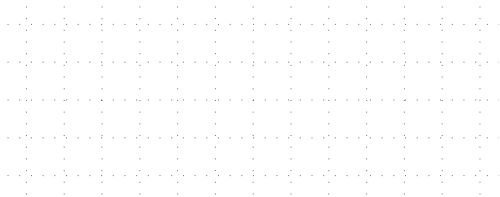

	S1 S0			
D	00	01	11	10
0				
1				



Problem 3. FSM Gate-Level Implementation

Draw the gate-level implementation of this FSM.

